
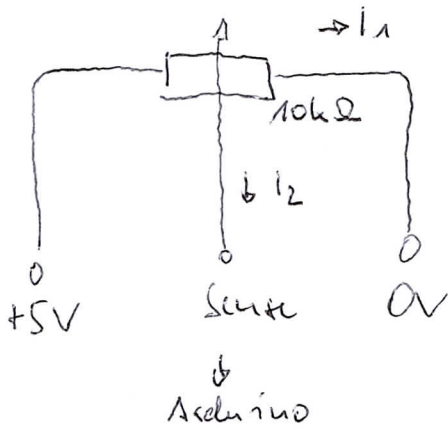


richtig - right

falsch - wrong

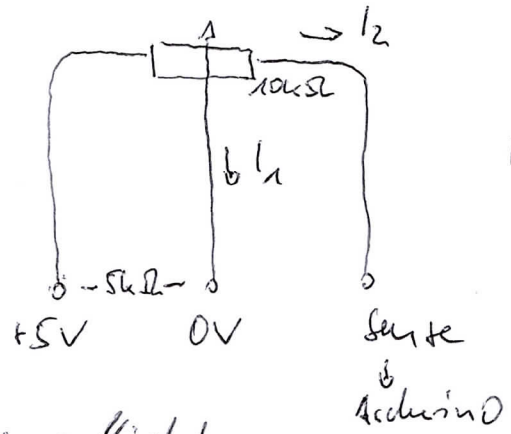


$I_1 \approx 0,5 \text{ mA}$
 $I_2 = 0 \text{ mA}$




$I_1 \approx 1 \text{ mA}$
 $I_2 = 0 \text{ mA}$

Mittelstellung - Middle

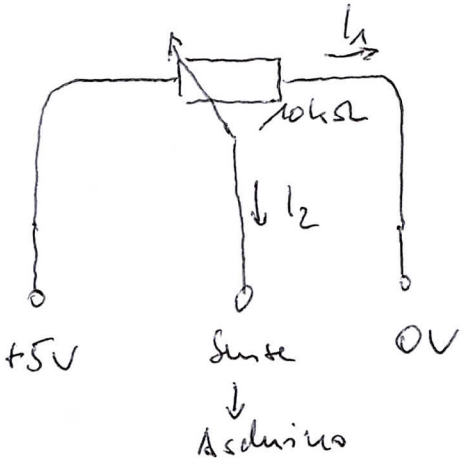


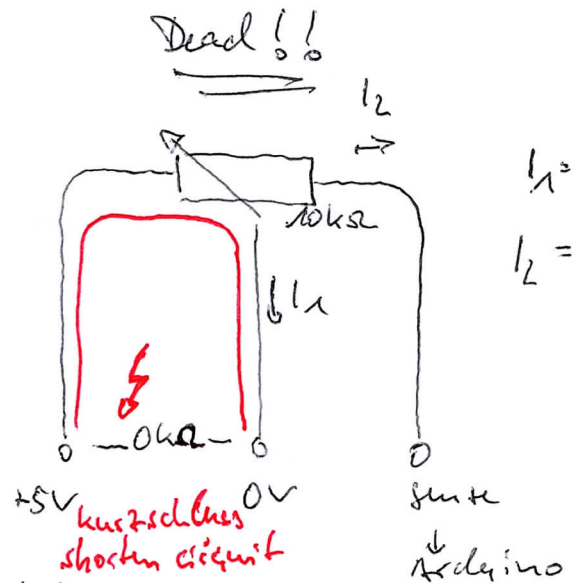$I_1 \approx 0,5 \text{ mA}$
 $I_2 = 0 \text{ mA}$




$I_1 = \text{max A}$
 $I_2 = 0 \text{ mA}$

Endstellung 1 - Endstop 1

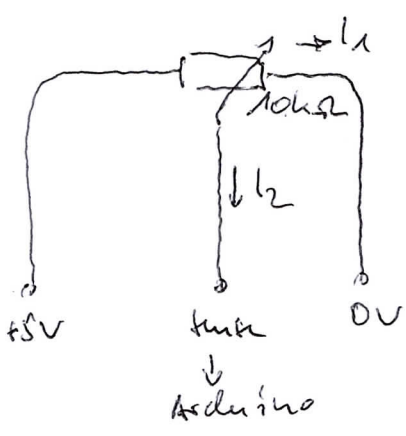

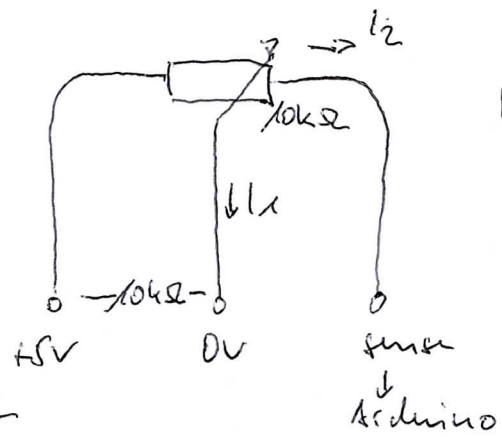$I_1 \approx 0,5 \text{ mA}$
 $I_2 = 0 \text{ mA}$



$I_1 \approx 0,5 \text{ mA}$
 $I_2 = 0 \text{ mA}$

Endstellung 2 - Endstop 2